

CHAPTER 5: PART II

Design Procedure of Sequential circuit

- i. Problem is stated
- ii. Obtain the state table
- iii. State reduction
- iv. Assign binary values to each state
- v. Determine the number of FFs needed (from the number of states) and assign a letter symbol to each
- vi. Choose the type of FF to be used (suggestions: for general application use JK FF, requiring transfer of data use SR/D FF, involving complementation use T FF)
- vii. Derive the excitation map
- viii. Derive the circuit output function and the FF input function
- ix. Draw the logic diagram

Analysis of Clocked Sequential Circuits: Terminology

- *State Equation*: A state equation (transition equation) specifies the next state as a function of the present state and inputs.
- *State Table*: A state table (transition table) consists of: present state, input, next state and output.
- *State Diagram*: The information in a state table can be represented graphically in a state diagram. The state is represented by a circle and the transitions between states are indicated by directed lines connecting the circles.