



# **CSE 2105: DIGITAL LOGIC DESIGN**

## **Combinational Logic**

## ○ Logic Circuits:

- Logic circuits for digital systems may be combinational or sequential.

## ○ Combinational Circuits:

- A combinational circuit consists of logic gates whose outputs at any time are determined directly from the **present combination of inputs without regard to previous inputs.**
- A combinational circuit consists of input variables, logic gates and output variables. The logic gates accept signals from the inputs and generate signals to the outputs.
- This process transforms binary information from the given input data to the required output data.
- Obviously both input and output data are represented by binary signals.

# COMBINATIONAL CIRCUITS

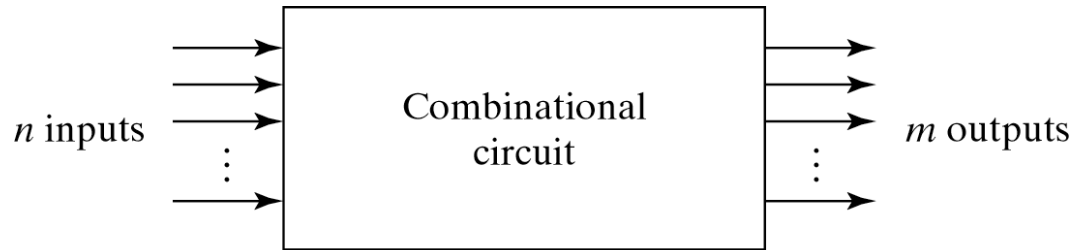



Fig. 4-1 Block Diagram of Combinational Circuit

- For  $n$  input variables, there are  $2^n$  possible combinations of binary input values. For each possible input combination, there is one and only one possible output combination.
- A combinational circuit can be described by  $m$  Boolean functions, one for each output variable.
- Each output function is expressed in terms of the  $n$  input variables.

## DESIGN PROCEDURE OF COMBINATIONAL LOGIC CIRCUIT

- Given a problem statement:
  - Determine the number of *input variables* and *output variables*. The input and output variables are assigned letter symbols.
  - Derive the truth table to define the required relationships between input and outputs.
  - Simplify the Boolean expression for each output.
  - Produce the required circuit and verify it.

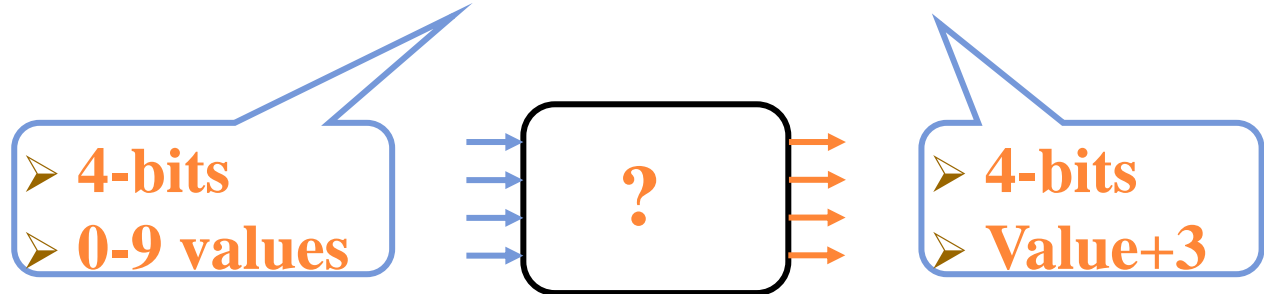
Example: Design a circuit to convert a 4 bit “BCD” digit to “Excess 3” code converter.




# DESIGN PROCEDURE

## BCD-TO-EXCESS 3 CONVERTER


<i>A B C D</i>	<i>w x y z</i>
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
1 0 1 0	x x x x
1 0 1 1	x x x x
1 1 0 0	x x x x
1 1 0 1	x x x x
1 1 1 0	x x x x
1 1 1 1	x x x x

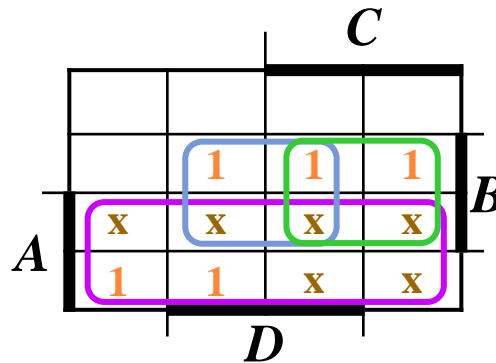


$$w = A + BC + BD$$

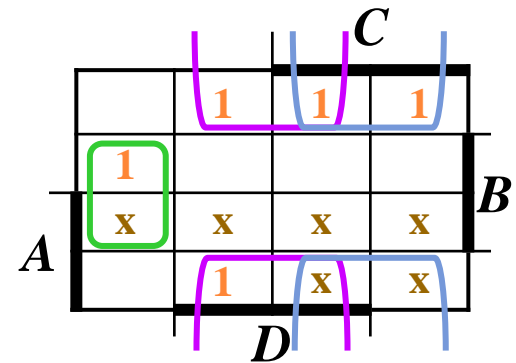

$$x = B'C + B'D + BC'D'$$

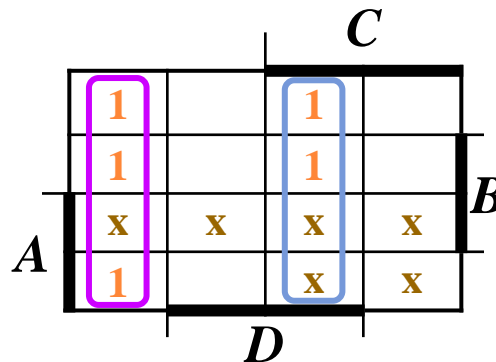

$$y = C'D' + CD$$

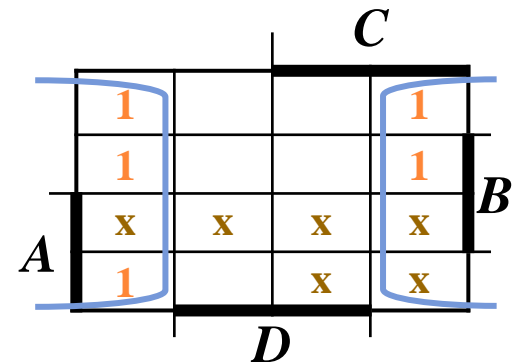


$$z = D'$$

# DESIGN PROCEDURE

## BCD-TO-EXCESS 3 CONVERTER

A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

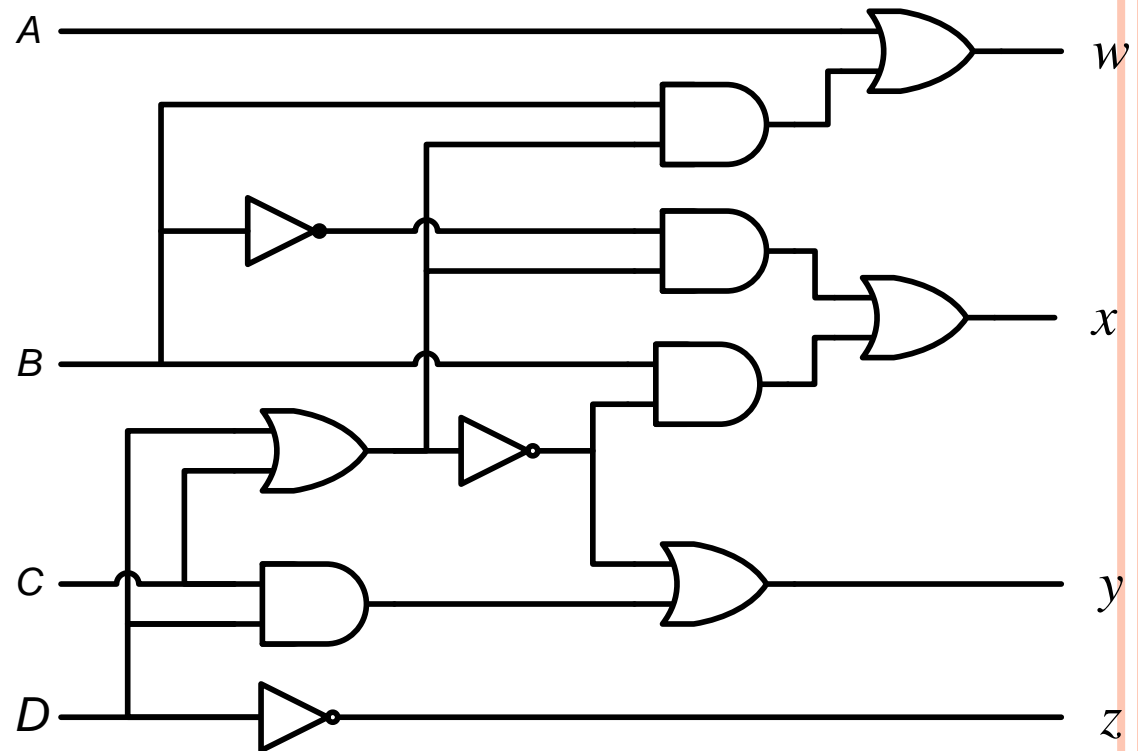

$$w = A + B(C+D)$$

$$x = B'(C+D) + B(C+D)'$$

$$y = (C+D)' + CD$$

$$z = D'$$

# VERIFICATION

Check the functional correctness of the logic circuit:

- Apply all possible input combinations
- And check if the circuit generates the correct outputs for each input combinations
- For large circuits with many input combinations, this may not be feasible.
- Statistical techniques may be used to verify the correctness of large circuits with many input combinations.

# EXERCISE

- Design a combinational circuit that converts a four bit Gray code to a four bit Binary number.
- Design a code converter that converts a decimal digit from the 8,4,-2,-1 code to BCD.
- Design a four bit 2's complementer circuit.
- Design a three bit square circuit.